

# Chapter 27

27-1

Storing the potential energy:




1 - Stretching a spring



2 - Compressing a gas




3 - lifting a mass

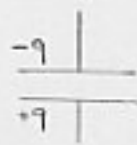

4 - Capacitor  
Potential energy  
in an electric  
field


27-2

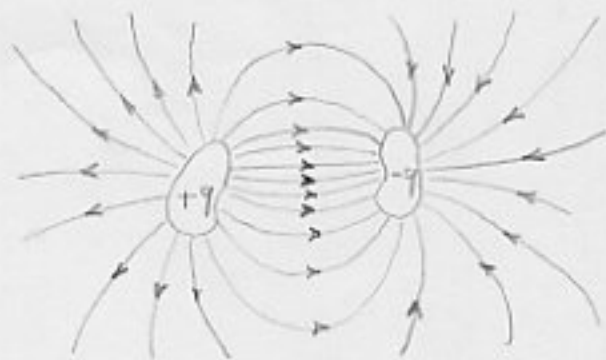Capacitor: Two isolated conductors of arbitrary shape carrying equal but opposite charges.



Charge of Capacitor:  $|q|$

Net charge of capacitor = 0

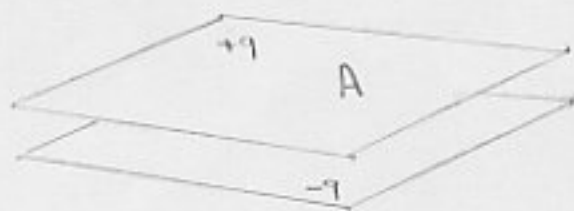


$\Delta V$ : Potential difference between the plates

$\Delta V$  For historical reasons is represented by  $V$

$$q \sim V$$

$$\rightarrow q = CV$$

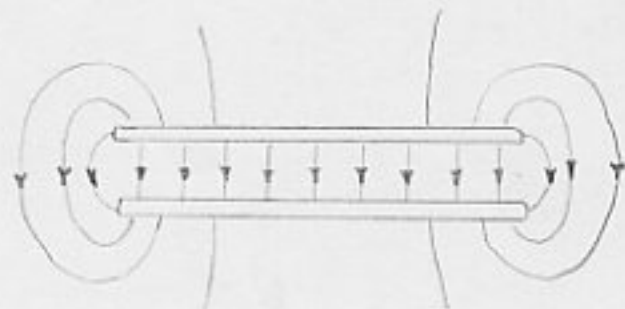

Parallel plate capacitor


$C = C$  (Geometry of the plates, insulators)

Capacitance

$$C: \frac{\text{Coulomb}}{\text{Volt}} = 1F \text{ (farad)}$$

SI unit

Charging a Capacitor:

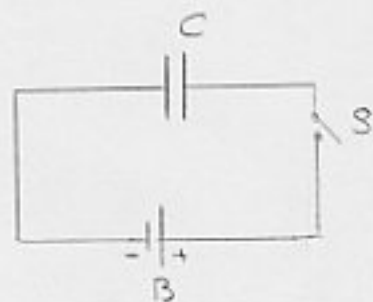

27-3 Calculating the Capacitance:

We follow 3-steps:

- 1- Assume a charge  $q$  on the plates
- 2- Calculate the electric field  $E$  between the plates
- 3- Knowing  $E$  calculate  $V$  and later  $C$ .

Calculating the electric field  $E$ :

$$\epsilon_0 \oint E \cdot dA = q$$

Calculating the Potential difference:

$$V_f - V_i = - \int_i^f E \cdot ds \quad V = \int^+ E \cdot ds \quad (V_f - V_i = -V)$$

(absolute value)

A parallel plate Capacitor:

We neglect the fringing of  $E$  at the edges of the plates.

$$\oint \vec{E} \cdot d\vec{A} = \frac{q}{\epsilon_0}$$

$$\int_1 + \dots + \int_6 = \frac{q}{\epsilon_0}$$

$$EA = \frac{q}{\epsilon_0} \quad E = \frac{q}{\epsilon_0 A}$$

$$V = \int_+^- \vec{E} \cdot d\vec{l} = E \int ds = Ed$$

$$V = \frac{qd}{\epsilon_0 A} \quad q = CV \quad q = C \frac{qd}{\epsilon_0 A} \quad C = \epsilon_0 \frac{A}{d}$$

→  $C = C(\text{Geometrical factors})$

## A cylindrical Capacitor

Assume  $L \gg b$  → we neglect the fringing of  $\vec{E}$  at the ends of cylinder



$$\oint \vec{E} \cdot d\vec{A} = \frac{q}{\epsilon_0}$$

$$(2\pi rL)E = \frac{q}{\epsilon_0} \quad E = \frac{q}{2\pi\epsilon_0 Lr}$$

$$V = \int_+^- \vec{E} \cdot d\vec{l} = \frac{q}{2\pi\epsilon_0 L} \int_a^b \frac{dr}{r}$$

$$= \frac{q}{2\pi\epsilon_0 L} \ln\left(\frac{b}{a}\right)$$
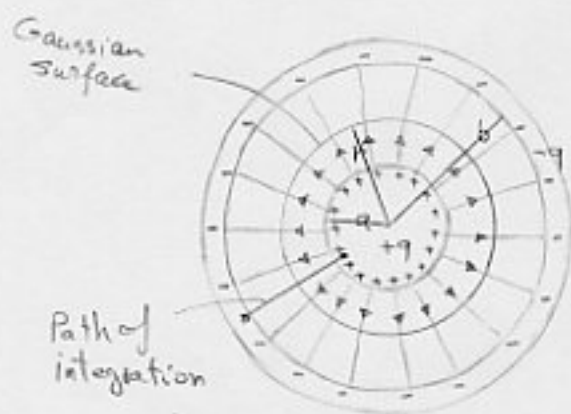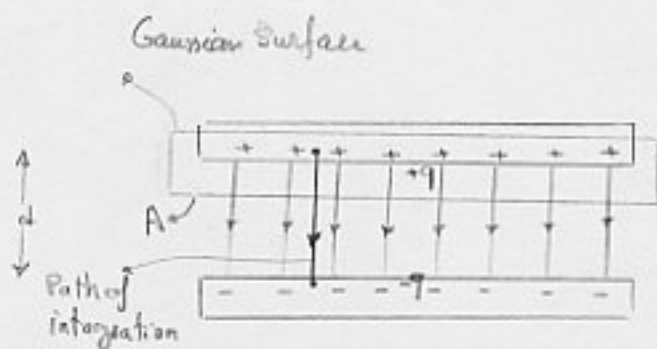
$$C = \frac{q}{V} \quad C = 2\pi\epsilon_0 \frac{L}{\ln\left(\frac{b}{a}\right)}$$



## A spherical Capacitor

$$\oint E \cdot dA = \frac{q}{\epsilon_0} \quad (4\pi r^2) E = \frac{q}{\epsilon_0}$$

$$E = \frac{1}{4\pi\epsilon_0} \frac{q}{r^2}$$

$$V = \int_+^- E \cdot dl = \frac{q}{4\pi\epsilon_0} \int_a^b \frac{dr}{r^2} = \frac{q}{4\pi\epsilon_0} \left( \frac{1}{a} - \frac{1}{b} \right)$$

$$V = \frac{q}{4\pi\epsilon_0} \frac{b-a}{ab} \quad C = 4\pi\epsilon_0 \frac{ab}{b-a}$$

## An isolated sphere:

We can assign a capacitance to a single isolated spherical conductor of radius  $R$  by assuming that the missing plate is a conducting sphere of infinite radius.

$$C = 4\pi\epsilon_0 \frac{a}{1 - \frac{a}{b}} \quad \begin{cases} b \rightarrow \infty \\ a = R \end{cases} \rightarrow C = 4\pi\epsilon_0 R$$

## Ex.

Parallel plate capacitor;  $d = 10 \text{ mm}$   $C = 1.0 \text{ F}$   $A = ?$

Sol.

$$A = \frac{Cd}{\epsilon_0} = \frac{(1.0 \text{ F})(10 \times 10^{-3} \text{ m})}{(8.85 \times 10^{-12} \text{ F/m})} = 1.1 \times 10^8 \text{ m}^2$$

## Ex

Coaxial cable,  $a = 0.15 \text{ mm}$   $b = 2.1 \text{ mm}$   $\frac{C}{L} = ?$

Sol.

$$\frac{C}{L} = \frac{2\pi\epsilon_0}{\ln\left(\frac{b}{a}\right)} = \frac{(2\pi)(8.85 \times 10^{-12})}{\ln\left(\frac{2.1}{0.15}\right)} = 21 \times 10^{-12} \text{ F/m} = 21 \text{ pF/m}$$

Ex.

$$C = 55 \text{ fF} \quad V = 5.3 \text{ V} \quad n = ? \text{ number of electrons}$$

Sol.

$$q = CV \quad n = \frac{q}{e} = \frac{CV}{e} = \frac{(55 \times 10^{-15})(5.3)}{1.6 \times 10^{-19}} = 1.8 \times 10^6 \text{ electrons}$$

Ex.

$C_{\text{Earth}} = ?$  as an isolating conducting sphere of radius 6370 km

Sol.

$$C = 4\pi\epsilon_0 R = (4\pi)(8.85 \times 10^{-12})(6.37 \times 10^6) = 7.1 \times 10^{-4} \text{ F} = 710 \text{ }\mu\text{F}$$

27-4 Capacitors in parallel and in series:

Capacitors in parallel:


(Fig. a)  $\approx$  (Fig. b) (i.e.  $q = q_1 + q_2 + q_3$ )  
equivalent

$$q_1 = C_1 V, \quad q_2 = C_2 V, \quad q_3 = C_3 V$$

$$q = q_1 + q_2 + q_3 = (C_1 + C_2 + C_3)V$$

$$C_{\text{eq}} = \frac{q}{V} = C_1 + C_2 + C_3$$

$$C_{\text{eq}} = \sum_{j=1}^n C_j$$

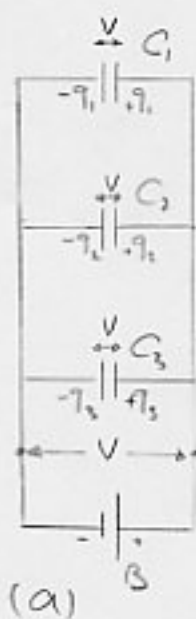

# Capacitors in Series:

$$V_1 = \frac{q}{C_1} \quad V_2 = \frac{q}{C_2} \quad V_3 = \frac{q}{C_3}$$



$$V = V_1 + V_2 + V_3 = q \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)$$

$$C_{eq} = \frac{q}{V} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C_{eq}} = \sum_{j=1}^n \frac{1}{C_j}$$

electrically isolated

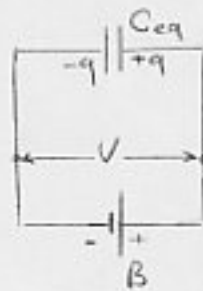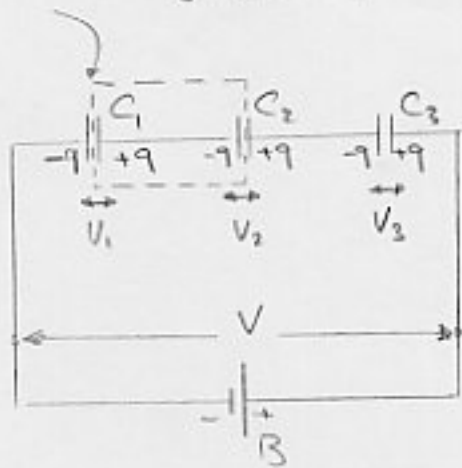

Ex.

$$C_1 = 12 \mu\text{F}, C_2 = 5.30 \mu\text{F} \quad C_3 = 4.5 \mu\text{F}$$

a)  $C_{eq} = ?$       b)  $V = 12.5$        $q_1 = ?$

Sol.

$$C_{12} = C_1 + C_2 = 17.3 \mu\text{F}$$




$$\frac{1}{C_{123}} = \frac{1}{C_{12}} + \frac{1}{C_3} = \frac{1}{17.3} + \frac{1}{4.5} = 0.280 \mu\text{F}^{-1}$$

$$C_{123} = 3.57 \mu\text{F}$$

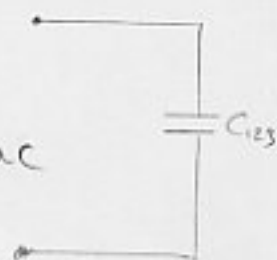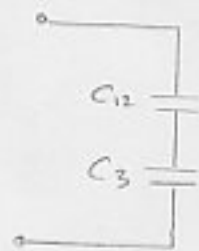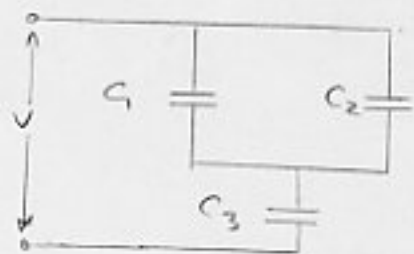b)  $q_{123} = C_{123} V = (3.57 \mu\text{F})(12.5 \text{V}) = 44.6 \mu\text{C}$

$$q_{123} = q_3 = q_{12} \quad V_{12} = \frac{q_{12}}{C_{12}} = \frac{44.6 \mu\text{C}}{17.3 \mu\text{F}} = 2.58 \text{V}$$

$$V_{12} = V_1 = V_2 \quad q_1 = C_1 V_1 = (12 \mu\text{F})(2.58 \text{V}) = 31 \mu\text{C}$$





Ex.

A 3.55 MF Capacitor  $C_1$  is charged to a potential difference  $V_0 = 6.30 \text{ V}$ . The battery is then removed and the capacitor is connected to an uncharged 8.95 MF capacitor  $C_2$ . What is the common potential difference?

Sol.

$$q_0 = q_1 + q_2 \rightarrow C_1 V_0 = C_1 V_1 + C_2 V_2 \quad (V_1 = V_2 = V)$$

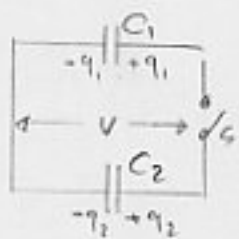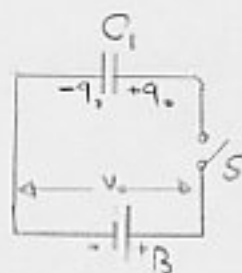
$$V = V_0 \frac{C_1}{C_1 + C_2} = \frac{(6.30 \text{ V})(3.55 \text{ MF})}{3.55 \text{ MF} + 8.95 \text{ MF}} = 1.79 \text{ V}$$



## 27-5 Storing Energy in an Electric Field:

Work must be done by an external agent to charge a capacitor.

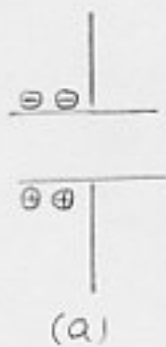
a) Suppose by some way we remove electrons from one plate and transfer them one at time to the other plate.



The  $E$ , build up in this way, tends to oppose further transfer.

Then, we have to do increasingly larger amount of work to transfer additional electrons.

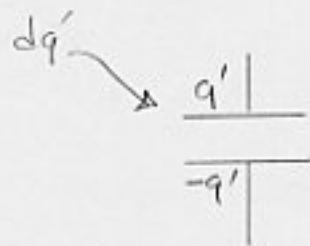Suppose at a given instant the charge of a plate is  $q'$ .



$$\rightarrow V' = \frac{q'}{C}$$

Now try to transfer extra  $dq'$  from one plate to that plate.

The required work is:

$$dW = V' dq' = \frac{q'}{C} dq'$$

$$W = \int dW = \frac{1}{C} \int_0^q q' dq' = \frac{q^2}{2C}$$

This work is stored as potential energy  $U$  in the capacitor:

$$U = \frac{q^2}{2C} \quad \rightarrow \quad U = \frac{1}{2} CV^2$$

Ex.

$C_1, C_2$  two parallel-plate capacitors with the same  $A$ , but  $C_2$  has twice separation of  $C_1$ .


$$C = \epsilon_0 \frac{A}{d} \rightarrow C_1 = 2C_2$$

If they have the same charge  $q$ ;  $q = \epsilon_0 EA \rightarrow E_1 = E_2$

$$U = \frac{q^2}{2C} \rightarrow U_2 = 2U_1 \quad (\text{Volume of } C_2 = 2 \text{ Volume of } C_1)$$

(Vol. between plates)

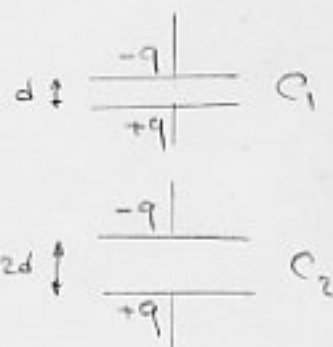$\rightarrow$  The potential energy of a charged capacitor may be viewed as stored in the electric field between its plates.





## Energy Density:

$$u = \frac{U}{\text{Volume}}$$

$$u = \frac{U}{Ad} = \frac{CV^2}{2Ad}$$

in parallel-plate capacitor.


(neglecting the fringing)  
 $u$  is uniform

$$C = \frac{\epsilon_0 A}{d} \rightarrow u = \frac{1}{2} \epsilon_0 \left(\frac{V}{d}\right)^2$$

$$\text{But } \frac{V}{d} = E \rightarrow u = \frac{1}{2} \epsilon_0 E^2 \quad (\text{it holds also in general})$$

Ex.  $C_1 = 3.55 \mu\text{F}$   $C_2 = 8.95 \mu\text{F}$   
 $V_0 = 6.30$

$U_i = ?$   $U_f = ?$

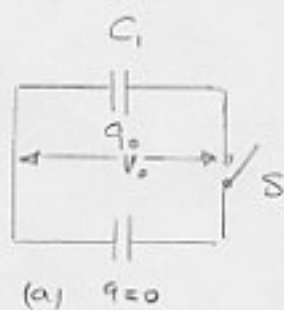

Sol.

$$U_i = \frac{1}{2} C_1 V_0^2 + 0 = \frac{1}{2} (3.55 \times 10^{-6} \text{ F}) (6.30)^2$$
$$= 70.4 \mu\text{J}$$


We found before  $V = 1.79 \text{ V}$

$$U_f = \frac{1}{2} C_1 V^2 + \frac{1}{2} C_2 V^2 = \frac{1}{2} (C_1 + C_2) V^2$$
$$= \frac{1}{2} (3.55 \times 10^{-6} + 8.95 \times 10^{-6}) (1.79)^2 = 20.0 \mu\text{J}$$

$$\rightarrow U_f < U_i \quad 72\%$$

This is not violation of Energy Cons.

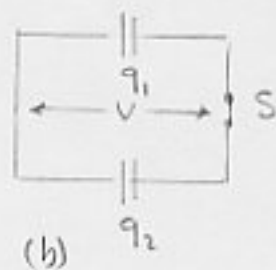The missing energy appears as radiation in the wires.



$$q_0 = q_1 + q_2$$

Ex.

$$R = 6.85 \text{ cm} \quad q = 1.25 \text{ nC}$$



Isolated Conducting Sphere

a)  $U = ?$  energy potential stored in the electric field

$$U = \frac{q^2}{2C} = \frac{q^2}{2(4\pi\epsilon_0 R)} = \frac{(1.25 \times 10^{-9} \text{ C})^2}{(8\pi)(8.85 \times 10^{-12} \text{ F/m})(0.0685 \text{ m})}$$

$$= 1.03 \times 10^{-7} \text{ J} = 103 \text{ nJ}$$

b)  $u = ?$  at the surface:

$$u = \frac{1}{2} \epsilon_0 E^2 \quad \text{Since } E = \frac{1}{4\pi\epsilon_0} \frac{q}{R^2} \quad u = \frac{1}{2} \epsilon_0 E^2 = \frac{q^2}{32\pi^2 \epsilon_0 R^4}$$

$$u = \frac{(1.25 \times 10^{-9} \text{ C})^2}{(32\pi^2)(8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2)(0.0685 \text{ m})^4} = 2.54 \times 10^{-5} \text{ J/m}^3 = 25.4 \text{ } \mu\text{J/m}^3$$

c) What is the radius  $R_0$  of an imaginary spherical surface such that one-half of the stored potential energy lies within it?

$$\int_R^{R_0} du = \frac{1}{2} \int_R^{\infty} du$$

$$\begin{cases} du = (u)(4\pi r^2)(dr) \\ u = \frac{1}{2} \epsilon_0 E^2 \quad \text{and } E = \frac{1}{4\pi\epsilon_0} \frac{q}{r^2} \end{cases} \rightarrow du = \frac{q^2}{8\pi\epsilon_0} \frac{dr}{r^2}$$

$$\rightarrow \int_R^{R_0} \frac{dr}{r^2} = \frac{1}{2} \int_R^{\infty} \frac{dr}{r^2} \rightarrow \frac{1}{R} - \frac{1}{R_0} = \frac{1}{2R}$$

$$R_0 = 2R = (2)(6.85 \text{ cm}) = 13.7 \text{ cm}$$

## 27-6 Capacitor with a Dielectric

1837, Michael Faraday (to whom the concept of capacitance is due, and for whom SI units of capacitance is named)

found that:

The capacitance increased by a factor  $k$  (dielectric const.) of the introduced material.

We have found before that  $C$  is always written in the form of

$$C = \epsilon_0 L \quad L: \text{has dimensions of length}$$

For example  $L = \frac{A}{d}$  for parallel plate capacitor

$$L = \frac{4\pi ab}{b-a} \text{ for spherical capacitor}$$

Faraday's discovery:

$$C = k\epsilon_0 L = k C_{\text{vacuum}}$$

for capacitors with dielectric

$$L = L(\text{Geometry})$$



$$C_2 = k C_1$$

# Faraday's Experiment:


a)  $V = \text{const.}$

$$C' = kC$$

$$V = \frac{q}{C} \quad V' = \frac{q'}{C'}$$

$$V = V' \rightarrow \frac{q}{C} = \frac{q'}{C'}$$
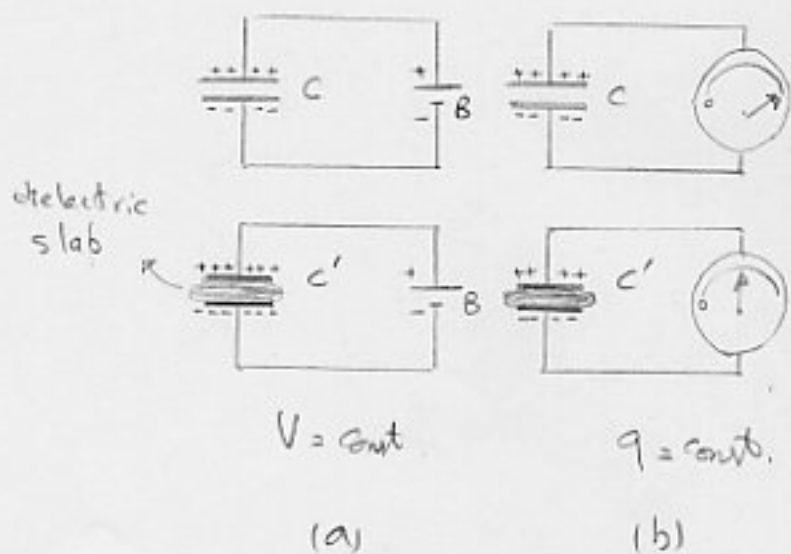
$$\frac{q}{C} = \frac{q'}{kC} \rightarrow q' = kq$$



b)  $q = \text{const.}$

$$q = CV \quad q' = C'V'$$

$$q' = q \rightarrow CV = C'V' \quad CV = kCV' \quad V' = \frac{V}{k}$$

Both experiments are consistent with  $C' = kC$

Thus;

In a region completely filled by a dielectric, all electrostatic equations containing the permittivity const.  $\epsilon_0$  are to be modified by replacing that const. to  $k\epsilon_0$ .

$$\epsilon_0 \rightarrow k\epsilon_0$$

For example;  $E = \frac{1}{4\pi\epsilon_0} \frac{q}{r^2} \rightarrow E = \frac{1}{4\pi k\epsilon_0} \frac{q}{r^2}$  (point charge)

Ex. A parallel-plate capacitor whose capacitance  $C$  is  $13.5 \text{ pF}$  has a potential difference  $V = 12.5 \text{ V}$  between its plates. The battery is now disconnected and a porcelain slab ( $K = 6.50$ ) is slipped between the plates. What is the potential energy of the device, both before and after the slab is introduced.

Sol.

$$U_i = \frac{1}{2} C V^2 = \frac{1}{2} (13.5 \times 10^{-12} \text{ F}) (12.5 \text{ V})^2 = 1.055 \times 10^{-9} \text{ J} = 1055 \text{ pJ}$$

$$U_i = \frac{q^2}{2C} \rightarrow U_f = \frac{q^2}{2C'} = \frac{q^2}{2kC} = \frac{U_i}{k} = \frac{1055 \text{ pJ}}{6.50} = 162 \text{ pJ}$$

$U_f$  is smaller by a factor of  $\frac{1}{k}$

Where has gone the missing energy?

This energy, in principle, would be apparent to the person who introduced the slab.

$$W = U_i - U_f = (1055 - 162) = 893 \text{ pJ}$$

If the slab were allowed to slide between the plates with no restraint and if there were no friction, the slab would oscillate back and forth between the plates with a constant mechanical energy  $893 \text{ pJ}$ .



## 27-7 Dielectrics: An Atomic View:

1-Polar dielectrics: The molecules of some dielectrics, like water have permanent electric dipole moments.



(a)  
 $E = 0$

The polar molecules have random direction

(b)  
 $E \neq 0$

The polar molecules tend to line up with  $E$ . Alignment increases with increasing  $E$  or decreasing  $T$  (thermal agitation decreasing)

2-Nonpolar dielectrics:

They acquire dipole moments in an external field.




(a)  
neutral molecules

(b)  
The presence of  $E_0$  stretch out the molecules and give the polarity

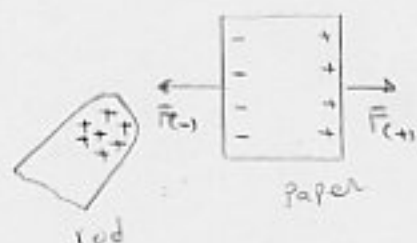(c)  
 $E'$  is produced by the molecules.  
 $E$ : resultant electric field

This is the origin of attraction of paper by the charged rod.



## 27-8 Dielectrics and Gauss' law

$$(a) \quad \epsilon_0 \oint E \cdot dA = \epsilon_0 E_0 A = q$$



$$E_0 = \frac{q}{\epsilon_0 A}$$

$$(b) \quad \epsilon_0 \oint E \cdot dA = \epsilon_0 E A = q - q'$$

$$E = \frac{q - q'}{\epsilon_0 A} \quad (1)$$

$q'$ : induced (bound) surface charge

$q$ : free charges on the plates

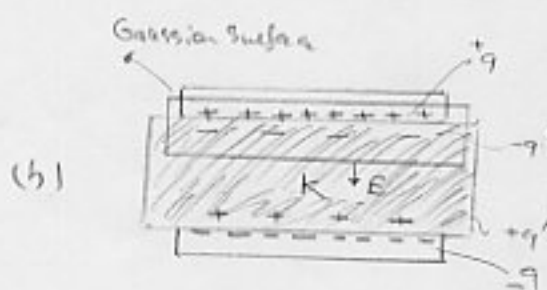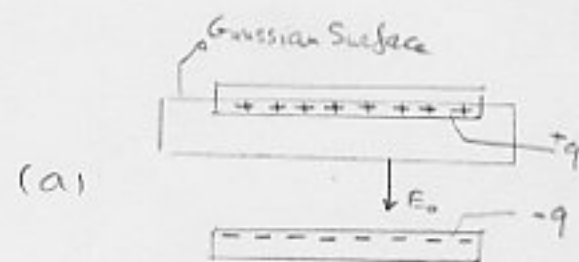

$$\text{Since } \epsilon_0 \rightarrow k\epsilon_0 \quad \Rightarrow \quad E = \frac{q}{k\epsilon_0 A} = \frac{E_0}{k} \quad (2)$$

$$(1), (2) \quad \Rightarrow \quad \frac{q - q'}{\epsilon_0 A} = \frac{q}{k\epsilon_0 A} \quad q - q' = \frac{q}{k}$$

$$\Rightarrow \begin{cases} q' < q \\ q' = 0 \text{ if } k=1 \end{cases}$$


$$\epsilon_0 \oint kE \cdot dA = q \quad (\text{Also valid generally})$$

$k = k(r)$  in general

$q$ : free charge only

Ex.

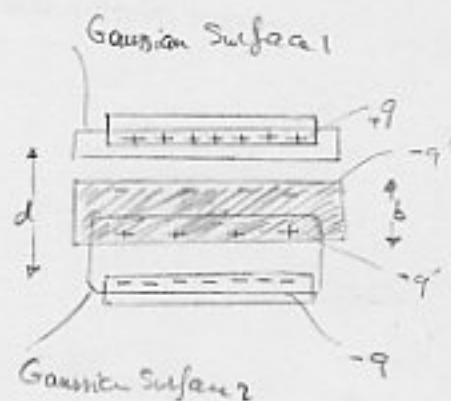The capacitor is charged and the battery is then disconnected and a dielectric slab is placed between the plates.



$$A = 115 \text{ cm}^2 \quad d = 1.24 \text{ cm}$$

$$b = 0.780 \text{ cm} \quad k = 2.61 \quad V_0 = 85.5 \text{ V}$$

a)  $C_0 = ?$

$$C_0 = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12} \text{ F/m})(115 \times 10^{-4} \text{ m}^2)}{1.24 \times 10^{-2} \text{ m}} = 8.21 \times 10^{-12} \text{ F} = 8.21 \text{ pF}$$

b)  $q = ?$  free charge

$$q = C_0 V_0 = (8.21 \times 10^{-12} \text{ F})(85.5 \text{ V}) = 7.02 \times 10^{-10} \text{ C} = 702 \text{ pC}$$

c)  $E_0 = ?$  in the gaps between the plates and the dielectric slab

$$\epsilon_0 \oint_{\text{Surface 1}} k E \cdot dA = q \quad \epsilon_0 (1) E_0 A = q$$

$$E_0 = \frac{q}{\epsilon_0 A} = \frac{7.02 \times 10^{-10} \text{ C}}{(8.85 \times 10^{-12} \text{ F/m})(115 \times 10^{-4} \text{ m}^2)} = 6900 \text{ V/m}$$

$E_0$  remains unchanged in the gap as the dielectric is introduced.

d)  $E' = ?$  in the dielectric slab.

$$\epsilon_0 \oint_{\text{Surface 2}} k E \cdot dA = q \quad -k \epsilon_0 E' = q$$



$$E' = \frac{q}{k\epsilon_0 A} = \frac{E_0}{k} = \frac{6900 \text{ V/m}}{2.61} = 2640 \text{ V/m}$$

e)  $V' = ?$

$$V' = + \int_{+}^{-} \vec{E} \cdot d\vec{s} = \int_{+}^{-} E ds = E_0 (d-b) + E' b$$

$$= (6900 \text{ V/m})(0.0124 \text{ m} - 0.00780 \text{ m}) + (2640 \text{ V/m})(0.00780 \text{ m}) = 52.3 \text{ V}$$

f)  $C' = ?$

$$C' = \frac{q}{V'} = \frac{7.02 \times 10^{-10} \text{ C}}{52.3 \text{ V}} = 1.34 \times 10^{-11} \text{ F} = 13.4 \text{ pF}$$

2E

The two metal objects in Fig. have net charges of  $+70 \text{ pC}$  and  $-70 \text{ pC}$  and this results a  $20 \text{ V}$  potential difference between them.



a)  $C = ?$

b) If the charges are changed to  $+200 \text{ pC}$  and  $-200 \text{ pC}$ , what does the capacitance become?

c) What does the potential difference become?

Sol.

a)  $q = CV$      $C = \frac{q}{V} = \frac{70 \times 10^{-12}}{20} = 3.5 \times 10^{-12} \text{ F}$

b) The same

c)  $V = \frac{q}{C} = \frac{200 \times 10^{-12}}{3.5 \times 10^{-12}} = 57 \text{ V}$

4E Show that the unit of  $\epsilon_0$ ,  $\frac{\text{F}}{\text{m}}$  and  $\frac{\text{C}^2}{\text{N}\cdot\text{m}^2}$  are equivalent.

Sol.

$$1 \text{ F} = 1 \frac{\text{C}}{\text{V}} \rightarrow \frac{\text{F}}{\text{m}} = \frac{\text{C}}{\text{V}\cdot\text{m}}$$

$$\text{But } 1 \frac{\text{N}}{\text{C}} = 1 \frac{\text{V}}{\text{m}} \rightarrow \text{V} = \frac{\text{N}\cdot\text{m}}{\text{C}}$$

$$\rightarrow \frac{\text{F}}{\text{m}} = \frac{\text{C}^2}{\text{N}\cdot\text{m}^2}$$

10E Two sheets of Al foil have a separation of 1.0 mm and a capacitance of 10 pF, and are charged to 12 V. a) calculate  $A = ?$

b)  $d$  is now changed to 0.1 mm with  $q = \text{const}$ .  $C_{\text{new}} = ?$

c)  $V_{\text{new}} = ?$

Sol.

$$a) C = \epsilon_0 \frac{A}{d} \quad A = \frac{Cd}{\epsilon_0} = \frac{(10 \times 10^{-12})(1 \times 10^{-3})}{8.85 \times 10^{-12}} = 1.13 \times 10^{-3} \text{ m}^2$$

$$b) C' = \epsilon_0 \frac{A}{d'} = 8.85 \times 10^{-12} \frac{1.13 \times 10^{-3}}{0.1 \times 10^{-3}} = 1 \times 10^{-10} \text{ F} = 100 \text{ pF}$$

$$c) q = CV = 10 \times 10^{-12} \times 12 = 1.2 \times 10^{-10} \text{ C}$$

$$q = C'V' \quad V' = \frac{q}{C'} = \frac{1.2 \times 10^{-10}}{1 \times 10^{-10}} = 1.2 \text{ V}$$

12P For a cylindrical capacitor we have,  $C = 2\pi\epsilon_0 \frac{L}{\ln \frac{b}{a}}$ .  
show that the capacitance approaches that of a parallel-plate capacitor when the spacing between the two cylinders is small.

Sol.

$$\ln(1+x) = x - \frac{1}{2}x^2 + \frac{1}{3}x^3 - \dots \quad (|x| < 1)$$

$$\rightarrow \ln(1+x) \approx x \quad (|x| < 1)$$

$$C = 2\pi\epsilon_0 \frac{L}{\ln \frac{b}{a}} = 2\pi\epsilon_0 \frac{L}{\ln \left(\frac{a+d}{a}\right)} = 2\pi\epsilon_0 \frac{L}{\ln \left(1 + \frac{d}{a}\right)}$$

$$C = 2\pi\epsilon_0 \frac{L}{\frac{d}{a}} \quad \left(\frac{d}{a} \ll 1\right) \quad C = \epsilon_0 \frac{(2\pi a)L}{d} = \epsilon_0 \frac{A}{d}$$

14P.

$$\text{Show that } \frac{dC}{dT} = C \left( \frac{1}{A} \frac{dA}{dT} - \frac{1}{x} \frac{dx}{dT} \right)$$


(T: temp.)

For parallel plate capacitor;

$$C = \epsilon_0 \frac{A}{x} \rightarrow \frac{dC}{dT} = \epsilon_0 \left( \frac{1}{x} \frac{dA}{dT} - \frac{A}{x^2} \frac{dx}{dT} \right)$$

$$\frac{dC}{dT} = \epsilon_0 \frac{A}{x} \left( \frac{1}{A} \frac{dA}{dT} - \frac{1}{x} \frac{dx}{dT} \right) = C \left( \frac{1}{A} \frac{dA}{dT} - \frac{1}{x} \frac{dx}{dT} \right)$$
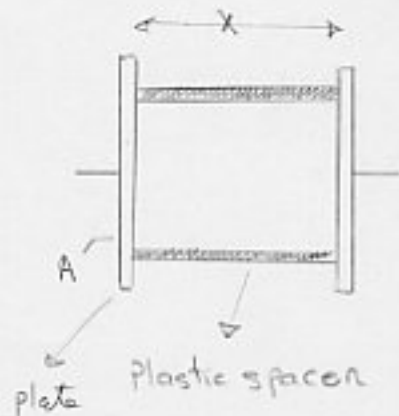
$$\frac{1}{A} \frac{dA}{dT} - \frac{1}{x} \frac{dx}{dT} = 0 \quad \text{cond. for } C = \text{const. (with changing T)}$$




15E.  $C_1 = 10.0 \text{ MF}$   $C_2 = 5.0 \text{ MF}$   $C_3 = 4.0$

$C_{\text{equ}} = ?$

$$C_{12} = C_1 + C_2 = 15 \text{ MF} \quad \frac{1}{C_{\text{eq}}} = \frac{1}{C_{12}} + \frac{1}{C_3}$$
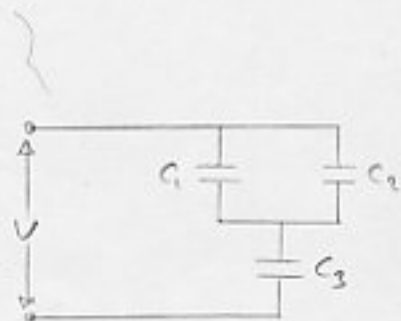
$$\rightarrow C_{\text{eq}} = 3.16 \text{ MF}$$




17E.  $C_1 = 10.0 \text{ MF}$   $C_2 = 5.0 \text{ MF}$   $C_3 = 4.0$

$C_{\text{equ}} = ?$

$$\frac{1}{C_{12}} = \frac{1}{C_1} + \frac{1}{C_2} \quad C_{12} = 3.33 \text{ MF}$$
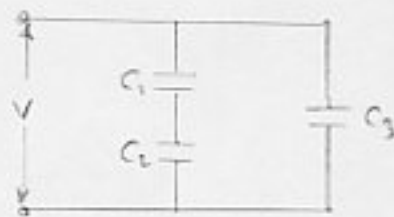
$$C_{\text{equ}} = C_{12} + C_3 = 7.33 \text{ MF}$$




26P

Show that  $C = \frac{\epsilon_0 A}{a-b}$  indep. of position  
of the center section.

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \quad C_1 = \epsilon_0 \frac{A}{a-b-x} \quad C_2 = \epsilon_0 \frac{A}{x}$$


$$\frac{1}{C} = \frac{a-b-x}{\epsilon_0 A} + \frac{x}{\epsilon_0 A} \quad \frac{1}{C} = \frac{1}{\epsilon_0 A} (a-b)$$

$$C = \epsilon_0 \frac{A}{a-b}$$

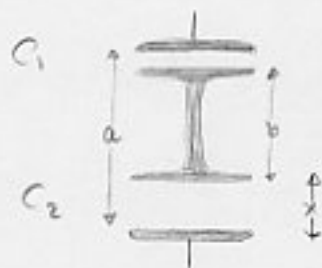

28P

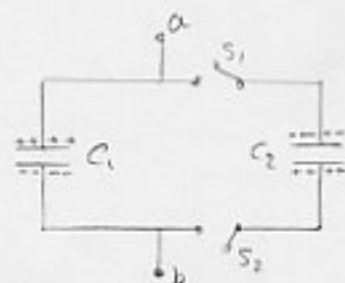$C_1 = 1.0 \mu\text{F}$  and  $C_2 = 3.0 \mu\text{F}$  are each charged to a potential  $V = 100 \text{ V}$  but with opposite polarity.



Switches  $S_1$  and  $S_2$  are now closed.

a)  $V_a - V_b = ?$  b)  $q_1 = ?$  c)  $q_2 = ?$

Sol.

$$q_1 = C_1 V_1 \quad q_1 = 1 \times 10^{-6} \times 100 = 10^{-4} \text{ C}$$

$$q_2 = C_2 V_2 \quad q_2 = 3 \times 10^{-6} \times 100 = 3 \times 10^{-4} \text{ C}$$


$$Q = q_2 - q_1 = 2 \times 10^{-4} \text{ C}$$

$$\begin{cases} V' = \frac{q_1'}{C_1} \\ V' = \frac{q_2'}{C_2} \end{cases} \rightarrow \frac{q_1'}{C_1} = \frac{q_2'}{C_2} \rightarrow q_1' = \frac{q_2'}{3}$$

$$\begin{cases} q_2' = 3q_1' \\ q_1' + q_2' = 2 \times 10^{-4} \end{cases} \rightarrow \begin{cases} q_1' = 0.5 \times 10^{-4} \text{ C} \\ q_2' = 1.5 \times 10^{-4} \text{ C} \end{cases}$$

$C_1$  is first charged. Then the S is connected to terminal 2.

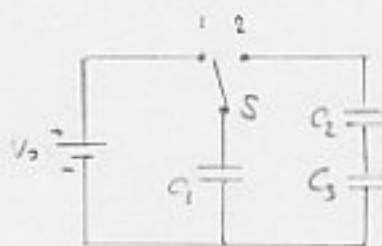What is final  $q_1 = ?$ ,  $q_2 = ?$ ,  $q_3 = ?$ .



Sol.

$$q_1 = C_1 V_0$$

$$\frac{1}{C_{23}} = \frac{1}{C_2} + \frac{1}{C_3} \rightarrow C_{23} = \frac{C_2 C_3}{C_2 + C_3}$$

$$\begin{cases} q_{23} = C_{23} V' \\ q_1' = C_1 V' \end{cases} \rightarrow \begin{cases} C_1 q_{23} = C_{23} q_1' \\ q_{23} + q_1' = q_1 = C_1 V_0 \end{cases} \quad C_1 q_{23} = C_{23} (C_1 V_0 - q_{23})$$

$$q_{23} + q_1' = q_1$$


$$q_{23} = \frac{C_{23} C_1 V_0}{C_1 + C_{23}} \rightarrow q_{23} = \frac{\frac{C_1 C_2 C_3}{C_2 + C_3} V_0}{C_1 + \frac{C_2 C_3}{C_2 + C_3}} \rightarrow q_{23} = q_2 = q_3$$

$$q_1' = C_1 V_0 - q_{23} = C_1 V_0 - \frac{\frac{C_1 C_2 C_3}{C_2 + C_3} V_0}{C_1 + \frac{C_2 C_3}{C_2 + C_3}} = \frac{C_1 C_2 C_3}{C_1 + C_2 C_3} V_0$$

64P

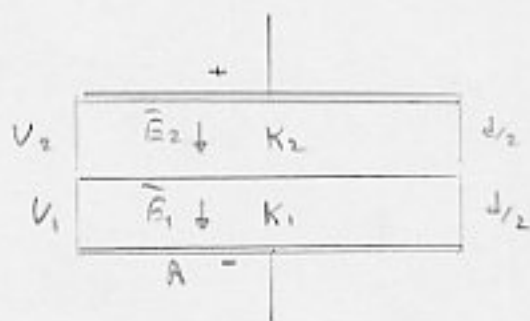a) Show that:

$$C = \frac{2\epsilon_0 A}{d} \left( \frac{k_1 k_2}{k_1 + k_2} \right)$$



b) Can you justify this arrangement as being two capacitors in series?

Sol:

$$a) E_1 = \frac{\sigma}{\epsilon_0 k_1} = \frac{q}{\epsilon_0 A k_1} \quad E_2 = \frac{\sigma}{\epsilon_0 k_2} = \frac{q}{\epsilon_0 A k_2}$$

$$V = \int E \cdot dl \quad V_1 = E_1 \frac{d}{2} \quad V_2 = E_2 \frac{d}{2}$$

$$V = V_1 + V_2 = (E_1 + E_2) \frac{d}{2} = \frac{q d}{2\epsilon_0 A} \left( \frac{1}{k_1} + \frac{1}{k_2} \right) = \frac{q d}{2\epsilon_0 A} \left( \frac{k_1 + k_2}{k_1 k_2} \right)$$

$$C = \frac{q}{V} = \frac{2\epsilon_0 A}{d} \left( \frac{k_1 k_2}{k_1 + k_2} \right)$$


b) Yes, since if we calculate;

$$C_1 = \frac{q}{V_1} = \frac{2\epsilon_0 A k_1}{d} \quad C_2 = \frac{2\epsilon_0 A k_2}{d}$$


$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \quad \rightarrow C = \frac{2\epsilon_0 A}{d} \left( \frac{k_1 k_2}{k_1 + k_2} \right)$$

If  $k_1 = k_2 = k \quad C = \epsilon_0 k \frac{A}{d}$

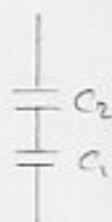If  $k_1 = k_2 = 1 \quad \rightarrow C = \epsilon_0 \frac{A}{d}$



GSP  $C = ?$

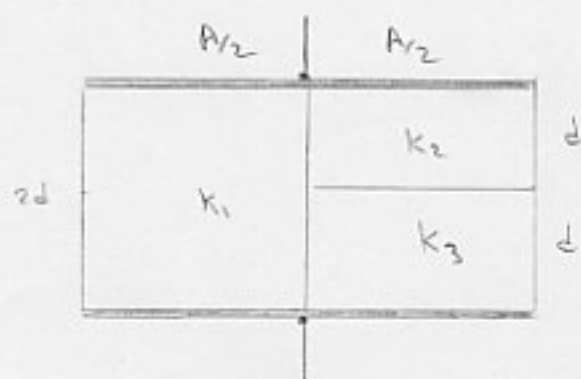


Sol.  $E = \frac{\sigma}{\epsilon_0 k} = \frac{q}{\epsilon_0 A k}$   $V = \int E \cdot dl$

$V = \frac{q d}{\epsilon_0 A k}$   $C = \frac{q}{V} = \frac{\epsilon_0 A k}{d}$

$C_1 = \frac{\epsilon_0 k_1 A/2}{2d}$   $C_2 = \frac{\epsilon_0 k_2 A/2}{d}$   $C_3 = \frac{\epsilon_0 k_3 A/2}{d}$

$C_{23} = \frac{C_2 C_3}{C_2 + C_3}$   $C_{23} = \frac{\epsilon_0 A}{2d} \left( \frac{k_2 k_3}{k_2 + k_3} \right)$

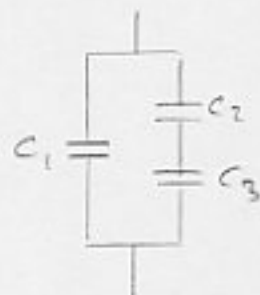$C_{eq} = C_{23} + C_1$   $C = \frac{\epsilon_0 A}{2d} \left( \frac{k_1}{2} + \frac{k_2 k_3}{k_2 + k_3} \right)$




GIP

a)  $C = ?$  after the copper slab is introduced.

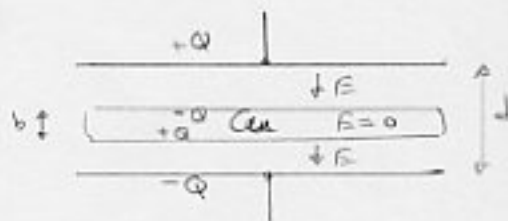b) If a charge  $q$  is maintained on the plate,

find  $\frac{U_0}{U} = ?$  c) Work done on slab = ?



Sol. a)  $C = \frac{\epsilon_0 A}{D}$   $C_1 = C_2 = \frac{\epsilon_0 A}{\frac{d-b}{2}}$

$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$   $C_{eq} = \frac{\epsilon_0 A}{d-b}$

b)  $U_0 = \frac{1}{2} \frac{q^2}{C}$   $C = \frac{\epsilon_0 A}{d} \rightarrow U_0 = \frac{d q^2}{2 \epsilon_0 A}$


$U = \frac{1}{2} \frac{q^2}{C_{eq}} = \frac{(d-b) q^2}{2 \epsilon_0 A}$

$\frac{U_0}{U} = \frac{d}{d-b}$

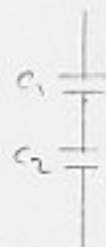c)  $U - U_0 = - \frac{b q^2}{2 \epsilon_0 A}$

Since  $U < U_0 \rightarrow$

The slab is sucked (system tends to reach Min. energy)






$$C_{xy} = ? \quad C_1 = C_2 = \dots = C_{12} = 10 \mu F$$

$$V_{xy} = \frac{q_1}{C_1} + \frac{q_1}{C_2} = \frac{2q_1}{10} = \frac{q_1}{5}$$

$$V_{xy} = \frac{q_2}{C_3} + \frac{q_2 - q_3}{C_4} + \frac{q_2}{C_5} = \frac{3q_2}{10} - \frac{q_3}{10}$$
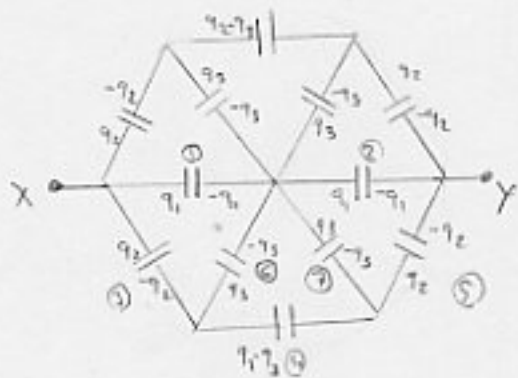
$$V_{xy} = \frac{q_2}{C_3} + \frac{q_3}{C_6} + \frac{q_1}{C_2} = \frac{q_2}{10} + \frac{q_3}{10} + \frac{q_1}{10}$$




$$\begin{cases} q_1 = 5V_{xy} \\ 3q_2 - q_3 = 10V_{xy} \\ q_1 + q_2 + q_3 = 10V_{xy} \end{cases}$$

$$\begin{cases} q_1 = 5V_{xy} \\ q_2 = \frac{5}{2}V_{xy} \\ q_3 = \frac{5}{2}V_{xy} \end{cases}$$

$$Q = q_1 + 2q_2 = 10V_{xy} \quad C_{xy} = \frac{Q}{V_{xy}} = \frac{10V_{xy}}{V_{xy}} = 10 \mu F$$

Ex 1

$C_{xy} = ?$

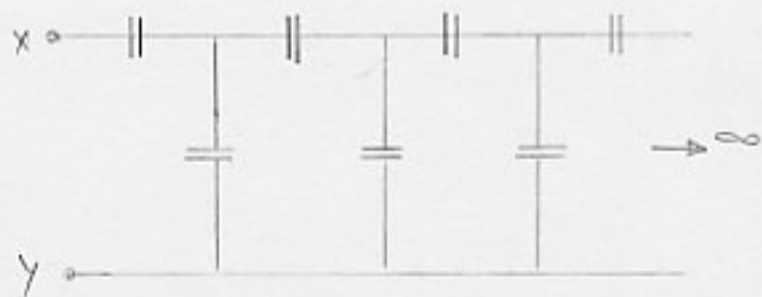

$C_{x_3 y_3} = \frac{8}{13} C$

$C_{x_2 y_2} = \frac{3}{5} C$


$C_{x_1 y_1} = \frac{C}{2}$

$\frac{1}{2} C < \frac{3}{5} C < \frac{8}{13} C < \dots < C$

$C_{xy} = C$

$n \rightarrow \infty$

Ex 2  $C_{xy} = ?$

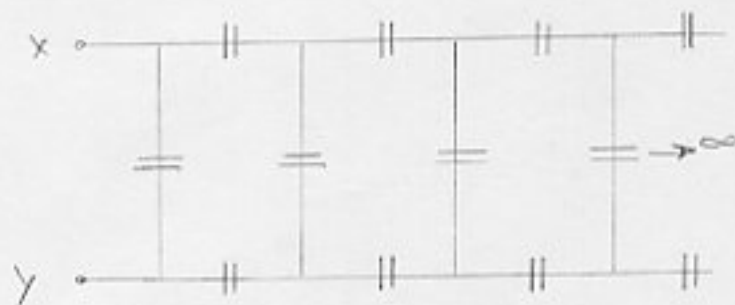

Similarly:

$\frac{C}{3} < \frac{4C}{11} < \frac{15C}{41} < \dots < C$

$C_{xy} = C + C = 2C$

