## Battery & resistor games

the problem solved in the tutorial. It is a well known problem in Physics and Engineering (although I don't have a precise reference for it).

The problem: Assume we have the DC circuit as sketched in Figure 1. The battery has the EMF

R

Figure 1: Circuit diagram for one battery + resistor

law for the loop. We have

$$\mathcal{E} = Ir + IR,\tag{1}$$

where I stands for the current through the circuit. The power delivered to R is given by

$$P_R = P(R) = I^2 R = \frac{\mathcal{E}^2 R}{(R+r)^2}.$$
 (2)

To solve the problem we apply Kirchhoff's At this point we can just simply take the derivative of P(R) with respect to R, set it to zero and solve for R. The function P(R) at the solution will have an extremum; to check that we have a maximum we would need to take the second derivative, P''(R) and see if it is negative when evaluate at the "suspect" point.



Figure 2: A sketch of the P(R) behaviour

It would be a bit more educating to proceed form at a slower pace, with a bit less mathematics (at least at the beginning). Let us first stare a bit at equation (2), which is now rewritten in the

$$P(R) = \frac{\mathcal{E}^2}{r^2} \frac{R}{\left(1 + \frac{R}{r}\right)^2}.$$
 (3)

Now, it becomes obvious that for  $R \to 0$  the

These notes are a wrapped-up version of  $\mathcal{E}$  and internal resistance r. The external resistor has resistance R which can be varied (from 0 to  $\infty$ ). The task: find the value of R for which the power  $P_R$  delivered to/dissipated on R reaches its maximum.

expression for  $P_R$  also goes to 0, and almost Here  $I_{short}$  stands for the shortcircuit current linearly (indeed, in the denominator we have  $(1 + R/r)^2 \approx 1$ , hence  $P_R \propto R$  in this regime). For  $R \to \infty$  the picture is different, but  $P_R \to 0$ as well. In this case the denominator may be approximated by  $(R/r)^2$ ; therefore, the P(R)behaves like  $R/(R/r)^2 \propto 1/R$ . The behaviour of P(R) in both extreme cases is sketched in Fig. 2. Clearly, there must be a value(s) of Rfor which P(R) reaches maximum.

To find the value of R for which  $P_R$  reaches the extremum we still need to do the math. The first derivative on "the top of the hill" has to vanish:

$$\frac{dP(R)}{dR} = \mathcal{E}^2 \frac{r-R}{(r+R)^3} = 0.$$
 (4)

The unique solution of the above equation is R = r. To convince yourself that this value provides a maximum for  $P_R$  you have to take the second derivative of P(R) and check it is negative when evaluated at R = r. This task is left to the reader.

For completeness, let us calculate the value of  $P_{max}$ . We have

$$P_R\Big|_{R=r} = \frac{1}{4}\frac{\mathcal{E}^2}{r} = \frac{1}{4}I_{short}^2 r.$$
 (5)

- this is the maximum current the battery can deliver.

One may complicate the problem by considering (see Fig. 3) two batteries connected in parallel and delivering power to a (variable) resistor R. The reader is again advised to perform the same task: find the condition R should obey for the power dissipated on it to reach its maximum. As an incentive here is the answer for the power:

$$P_R = \frac{\left(\frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2}\right)^2}{\left(1 + R\left(\frac{1}{r_1} + \frac{1}{r_2}\right)\right)^2}R.$$
 (6)

The power is maximum when

$$R = r_e = \frac{r_1 r_2}{r_1 + r_2} \tag{7}$$

and the expression for the maximum power is similar to (5), with r being replaced by  $r_e$  and  $I_{short}$  being now the sum of the shortcircuit currents.



Figure 3: The circuit for the 2 batteries + resistor case