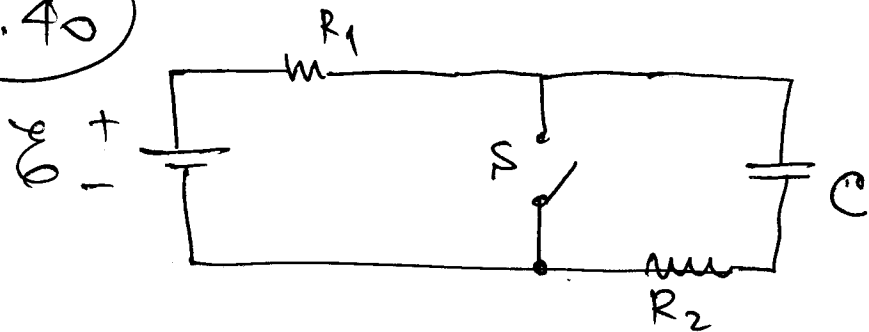


21.40




$$C = 10 \mu F$$

$$V = 10V$$

$$R_1 = 50 \text{ k}\Omega$$

$$R_2 = 100 \text{ k}\Omega$$

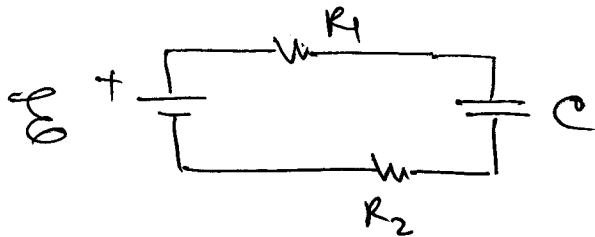(a) before S_1 is closed the circuit looks like




where R_1, R_2 are
in series

from the point of view
of C and E

$$\Rightarrow R_{\text{total}} = R_1 + R_2 = 150 \text{ k}\Omega$$

$$\tau_a = RC = 150 \cdot 10^3 \Omega \cdot 10 \cdot 10^{-6} F = 1.5 \text{ sec}$$

(6) after " S^4 " is closed we get:

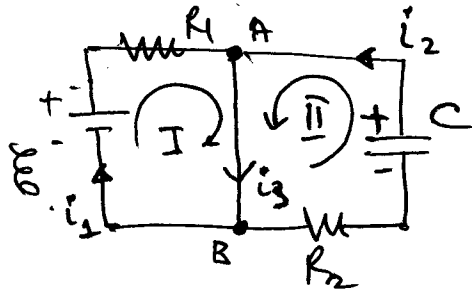

A and B have the same potential and therefore loop I does not feel II and vice-versa.

The time constant for 'C' branch is

$$\tau_b = R_2 C \approx 1 \text{ sec}$$

$$(c) \int \mathbf{r}_3 = \mathbf{r}_1 + \mathbf{r}_2$$

$$x = R_1 e_1$$

$$u_c = R_2 i_2$$

But $\mu_c = \mu_0 e^{-t/\tau_b}$

$$\leq \varepsilon \text{ (since charging was up to } \varepsilon)$$

(A)

(I)

(II)

$$\rightarrow i_3 = \frac{V_0}{R_1} + \frac{V_0 e^{-t/R_2 C}}{R_2}$$